

HDL, RTL and FPGA: Lab 1

Your first step in designing digital hardware

The informal explanation of acronyms

- HDL - Hardware Description Language
 - A language to design, simulate and verify circuits. We will use Verilog-2001.
- RTL - Register Transfer Level
 - A methodology to describe a circuit using HDL in a way that allows semi-automated conversion of the code into a blueprint for a physical chip manufactured on a foundry
- ASIC - Application-Specific Integrated Circuit
 - An example of ASIC is a chip that runs Android on your smartphone
- SoC - System on Chip
 - An ASIC that has one or several processor cores, memories and other components that form the whole computer system on a single chip
- FPGA - Field-Programmable Gate Array
 - A reconfigurable chip we will use as a substitute for manufacturing an ASIC


Hardware/software dualism - an informal example

Microcontroller (embedded chip, ASIC, SoC)

CPU

Designed
in Verilog

Executes
instructions

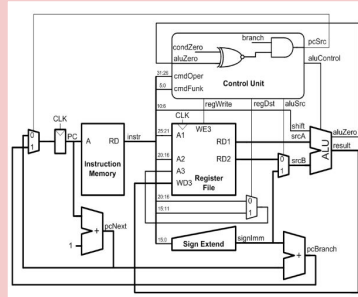


Memory

Contains a program,
a sequence of instructions

Compiled from C
or a similar language

```
18800005
00001025
00451021
0044182a
5460fffe
00451021
03e00008
00000000
```

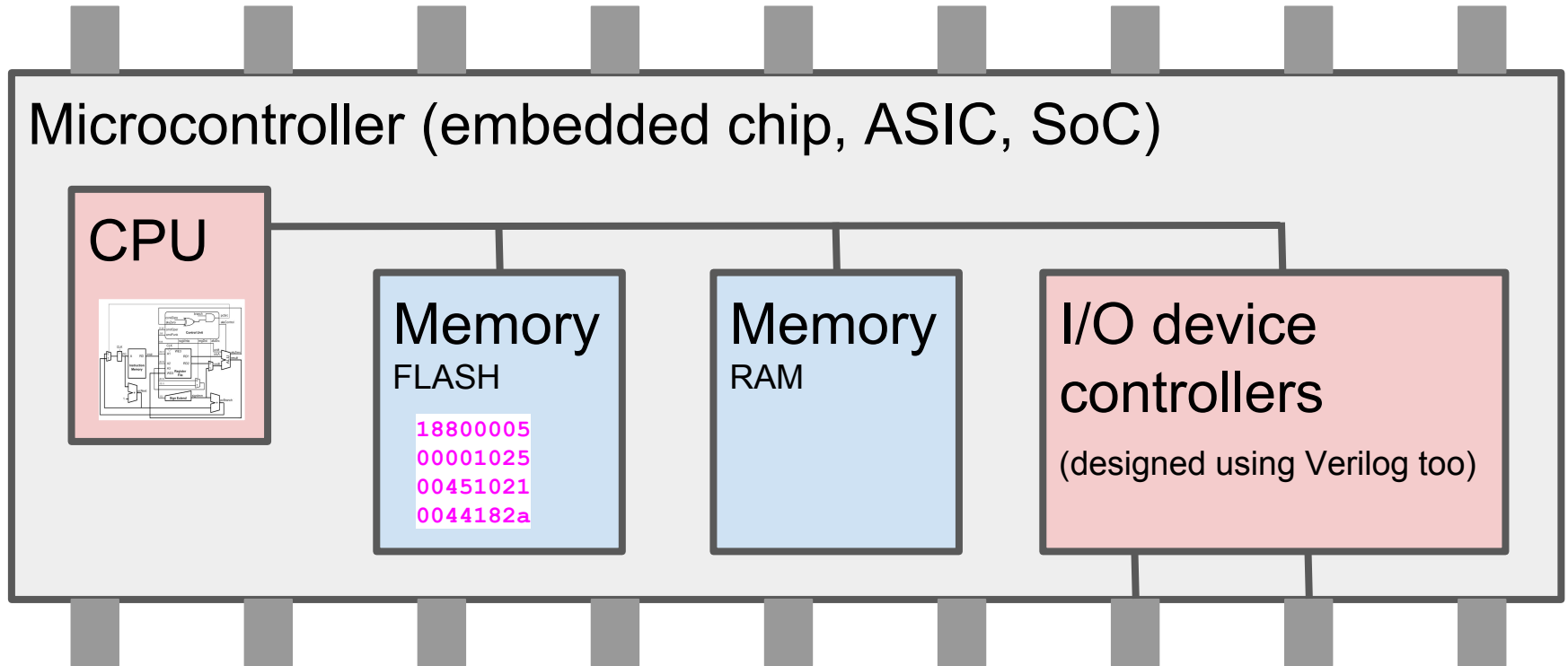Hardware/software dualism - an informal example / 2





Software: from C to processor instructions

C:	Assembly:	Machine code
<pre>int f (int a, int b) { int s = 0; while (s < a) s += b; return s; }</pre>	<pre>sum: blez \$4, exit move \$2, \$0 addu \$2, \$2, \$5 loop: slt \$3, \$2, \$4 bnel \$3, \$0, loop addu \$2, \$2, \$5 exit: jr \$31 nop</pre>	<pre>18800005 00001025 00451021 0044182a 5460ffffe 00451021 03e00008 00000000</pre>

Circuits: from Verilog to transistors (simplified)
  
```
module counter
(
  input clock,
  input reset,
  output logic [1:0] n
);
always @(posedge clock)
begin
  if (reset)
    n <= 0;
  else
    n <= n + 1;
end
endmodule
```




What is an FPGA? A simplified explanation

A matrix of cells with changeable function

One cell can become AND, another OR, yet another - one bit of memory

An FPGA does not contain a fixed CPU, but can be configured to work as a CPU

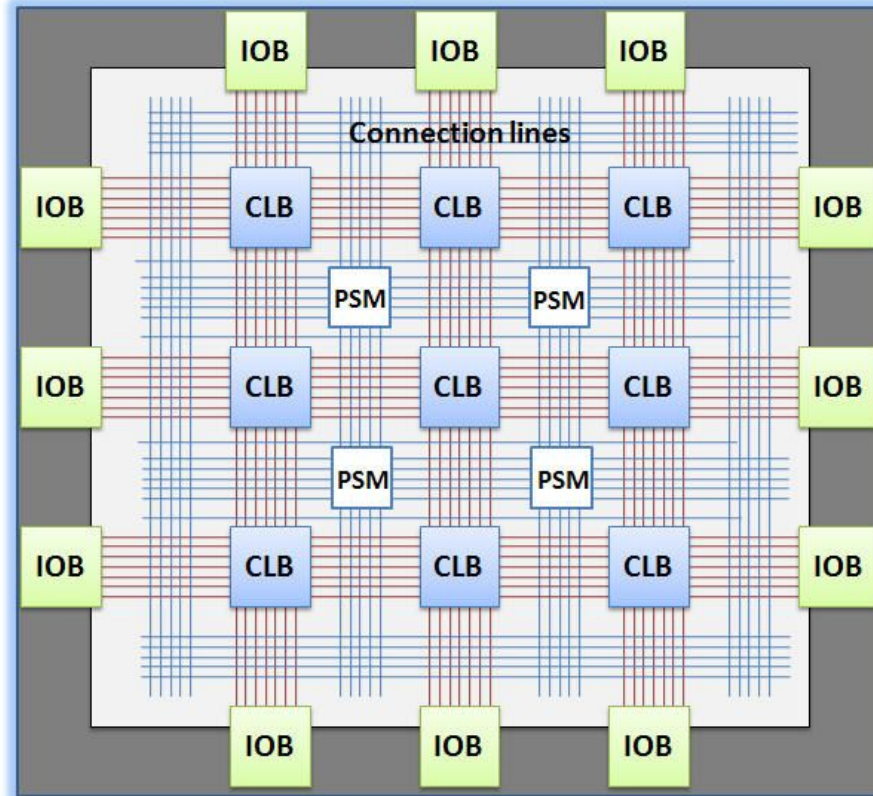A picture from
<http://jjmk.dk/MMMI/PLDs/FPGA/fpga.htm>



IOB
Input Output Block

CLB
Configurable
Logic Block

PSM
Programable
Switch Matrix

Connection lines
Single, Long
Double, Direct

What is inside an FPGA cell?



Each cell has multiplexers or muxes

A mux is a device that implements choice: “if ” in hardware

Muxes are connected to bits of memory, loaded from outside the FPGA

This allows forming circuits inside an FPGA by changing the contents of configuration memory

  Pictures are from <https://breadboardgremlins.wordpress.com/what-is-an-fpga/> and <http://www2.engr.arizona.edu/~rlysecky/courses/cs168-04w/lab7/lab7.html>



Twelve basic ideas of digital hardware design

- Gate

- Area

- Delay

- Parallelism

- Module

- Testbench

- Clock

- Reset

- D-Flip-Flop

- Power

- Finite State Machine

- Pipeline


We color-code the topics of Lab 1 in green, the topics of Lab 2 in blue and the topics of Lab 3 in purple.

A hardware design can be partitioned into

- Combinational logic
 - Used to calculate logic and arithmetical functions
- Sequential logic
 - Allows hardware to have memory and repeat actions
- The first lab covers only combinational logic

Combinational logic

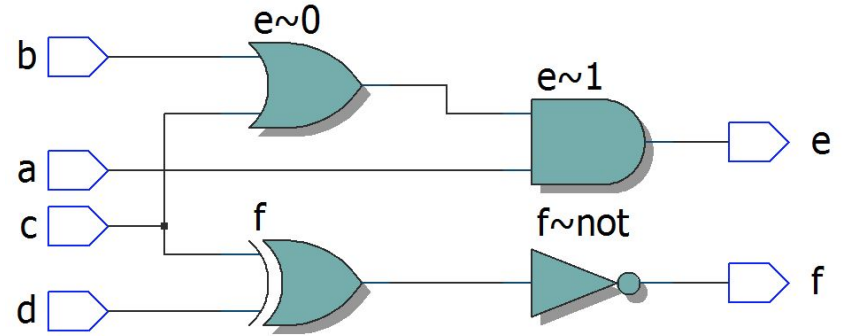- The outputs of the group of components depend only on inputs
- You set inputs and get outputs after some time
- This group is called “a combinational cloud”
- Used to calculate logic and arithmetical functions





```
module top
(
    input  a, b, c, d,
    output e, f
);

    assign e = a & (b | c);
    assign f = ~ (c ^ d);

endmodule
```

Sequential logic

 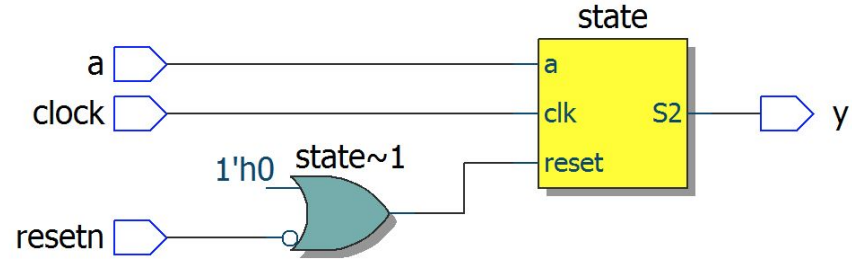- The outputs of the partition depend not only on inputs but also on internal state, stored in registers
- Change of the state is synchronized by a clock signal
- Allows hardware to be smart - memorize the intermediate results and iterate



Lab 1 exercises

1. Simulating a combinational module
 - a. Ports, continuous assignments, testbench, delay, waveforms
 - b. We will use ModelSim PE Student Edition from Mentor Graphics
2. Synthesizing a combinational module with basic gates
 - a. Logic synthesis, constraints, synthesized schematics, FPGA configuration
 - b. We will use Intel Quartus Lite Edition and Terasic DE10-Lite FPGA boards
3. Homework: Synthesize a combinational module that uses input from a button and muxes to output either your first name or last name to a multi-digit 7-segment indicator


Clone a repository from GitHub

Organization

<https://github.com/MIPSfpga>

Repository

digital-design-lab-manual

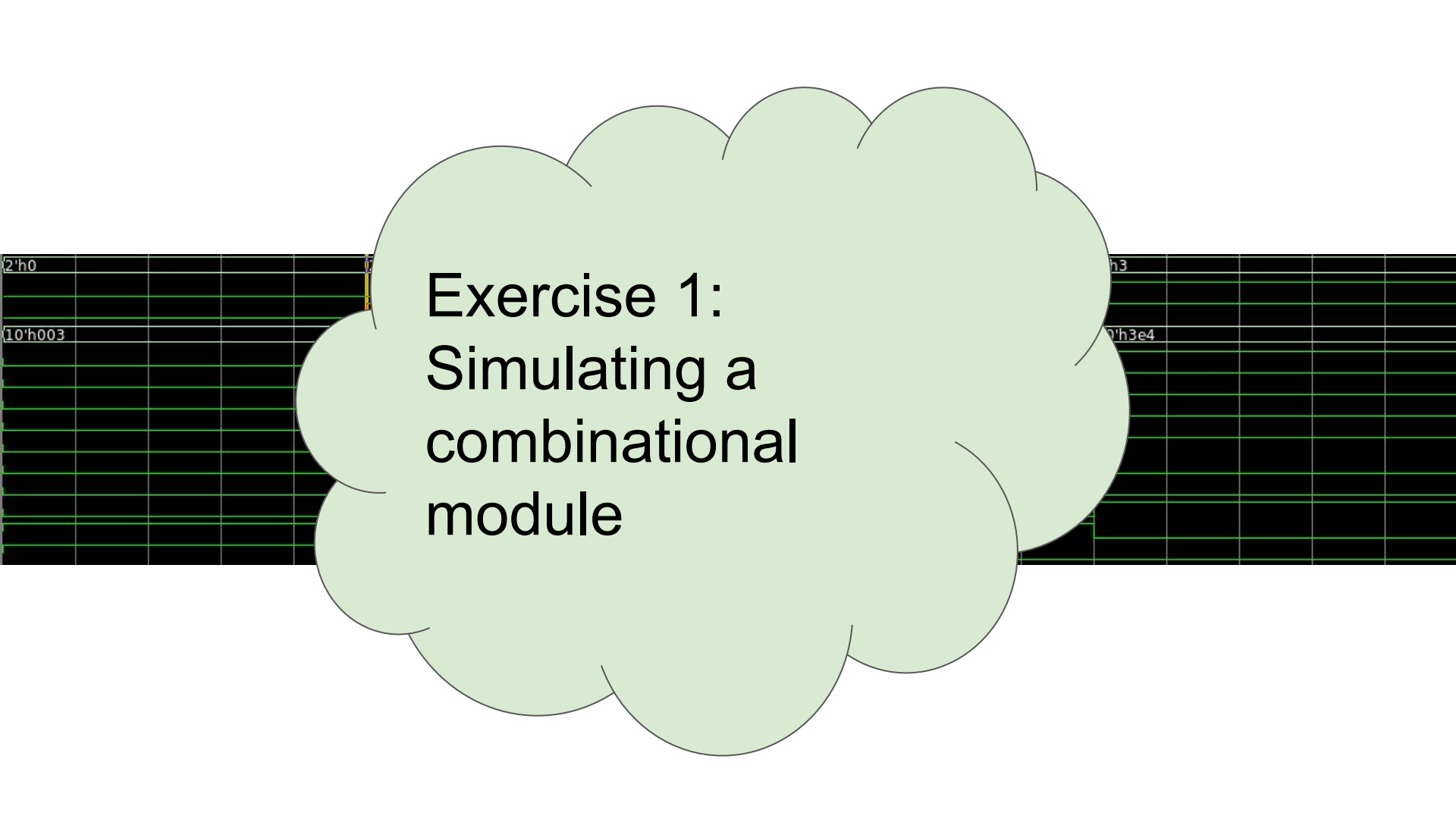

**Exercise 1:
Simulating a
combinational
module**

The design module - 1

- lab_01/src/lab1_hdl/lab1.v
- The unit of design is called “module”
- Module has a name and a list of ports
- Each port has a direction
 - input, output or inout
- Each port has a width / vector dimension
 - “[9:0]” means “10 bits from LED [9] through LED [0]”
 - If no dimension, 1-bit port assumed, such as “input ABC”

```
module lab1
(
    input [1:0] KEY,
    output [9:0] LED
);
```


The design module - 2

```
wire a = ~ KEY [0];
```

```
wire b = ~ KEY [1];
```

- lab_01/src/lab1_hdl/lab1.v
- “wire” declaration creates an intermediate connection between ports, other wires or “reg” variables to be discussed further
- wire can be 1-bit wide, or multiple bit wide, like “wire [4:0] A”
- The assignments to wires are continuous
 - Every time the expression on right hand side changes, it triggers change of the wire on left hand side
- Wires can be optimized away by the synthesis software

The design module - 3


```
// Basic gates AND, OR and NOT  
assign LED [0] = a & b;  
assign LED [1] = a | b;  
assign LED [2] = ~ a;
```

- lab_01/src/lab1_hdl/lab1.v
- The keyword “assign” is used for continuous assignments to an already declared port or a wire
- Note that the assignments do not assume a specific order - they semantically happen whenever the right hand side changes
- The HDL simulator is event-driven, it schedules the assignment evaluations by putting them into a queue of events
- HDL synthesis simply creates a netlist (graph) for an electric circuit

The simulation testbench - 1

- lab_01/src/lab1_hdl/simulation/testbench.v
- The testbench module (TB) is for simulation only, it is never synthesized
- TB contains a special program that tests the design module
- The design module instantiated inside TB is frequently referred to as DUT, Design under Test


```
module testbench;
```

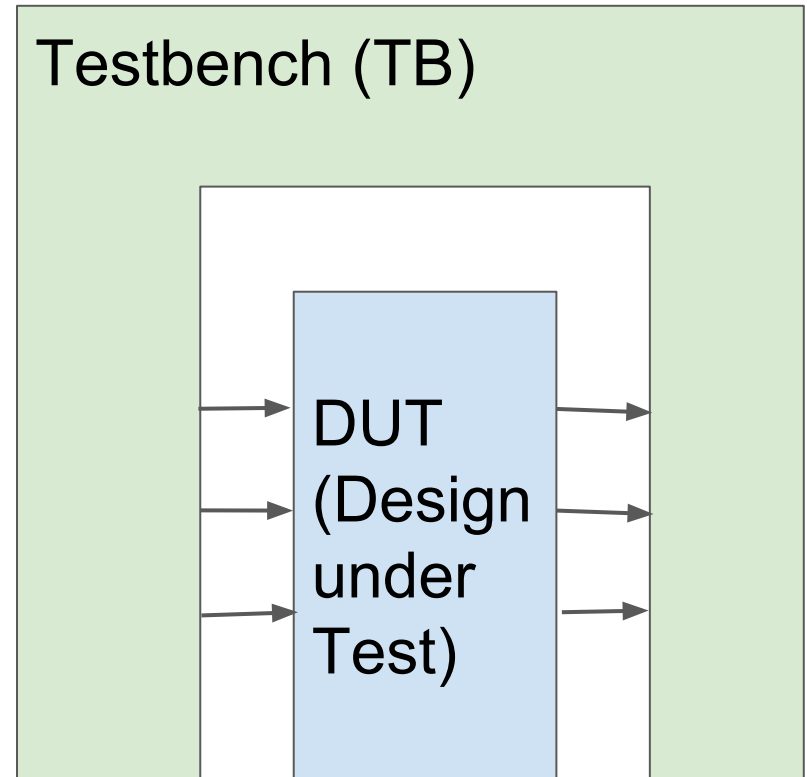

The simulation testbench - 2

```
module testbench;
```

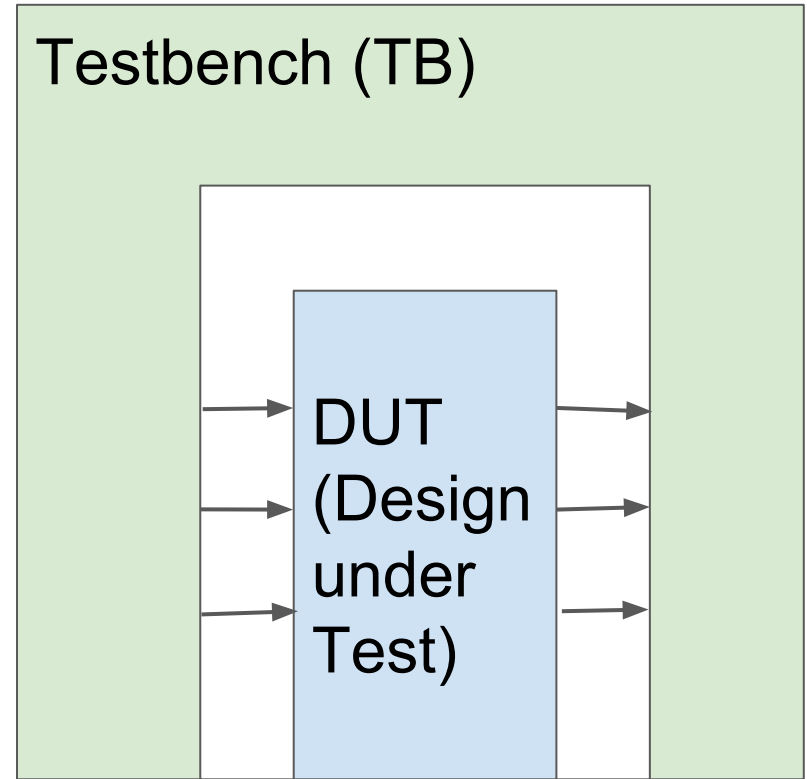- lab_01/src/lab1_hdl/simulation/testbench.v
- Testbench
 - Instantiates Design under Test
 - Drives stimulus
 - Checks the responses
- Testbench may also call functions in other languages (like C) to make verification environments more sophisticated



The simulation testbench - 3

- Module instantiation connects the design module's ports to the variables declared in the testbench
- Module instantiation looks like a function call, but it is not.
 - The DUT instance is physically put inside the testbench module
 - The connections between TB variables and DUT ports are continuous, just like the left and right sides of “assign”.

- lab_01/src/lab1_hdl/simulation/testbench.v

```
// input and output test signals
reg  [1:0] key;
wire [9:0] led;

// creating the instance of the
// lab1 - module name
// dut - instance name ('dut')
lab1 dut ( key, led );
```

The simulation testbench - 4

- lab_01/src/lab1_hdl/simulation/testbench.v
- Our TB generates stimulus in the simplest way:
 - Assign a value to a variable connected to DUT input port
 - Wait using #delay construct that causes simulator to postpone the execution of the next statement for a number of specified time units

```
initial
begin
    key = 2'b00;
    #10;
    key = 2'b01;
    #10;
    key = 2'b10;
    #10;
    key = 2'b11;
    #10;
end
```

The simulation testbench - 5

- lab_01/src/lab1_hdl/simulation/testbench.v
- Keyword “initial” means that the next statement is executed at the beginning of the simulation.
- “begin/end” means that the statements inside are executed sequentially.
- The assignments denoted with “=” inside “begin/end” are called “blocking assignments”. They are executed sequentially, not in parallel (“block the execution”).

```
initial
begin
    key = 2'b00;
    #10;
    key = 2'b01;
    #10;
    key = 2'b10;
    #10;
    key = 2'b11;
    #10;
end
```

The simulation testbench - 6

- lab_01/src/lab1_hdl/simulation/testbench.v
- The constant `2'b10` means “two bit-wide binary number 10”.
- The time unit in `#10` and simulation precision can be specified using ``timescale` directive. We will see this time later on simulation waveforms. If we put this directive at the beginning of the file, `#10` means “10 nanoseconds”:

```
`timescale 1 ns / 100 ps
```

```
initial
begin
    key = 2'b00;
    #10;
    key = 2'b01;
    #10;
    key = 2'b10;
    #10;
    key = 2'b11;
    #10;
end
```


The simulation testbench - 7

- lab_01/src/lab1_hdl/simulation/testbench.v
- `reg` declaration means “a variable that can be assigned inside a begin/end block”
- `$monitor` statement in initial block tells the simulator to print the specified text into the simulation log whenever any of the variables change

```
reg [1:0] key;
```

```
initial
```


```
$monitor("key=%b led=%b", key, led);
```

The simulation testbench - 8

`initial`

`$dumpvars;`

 - lab_01/src/lab1_hdl/simulation/testbench.v
- `$dumpvar` statement in initial block tells the simulator to generate the simulation waveforms.
- A waveform is a database of signal changes for debugging the design.
- The waveform can be viewed in a waveform viewer, either standalone (an example: GTKWave), or integrated into a Verilog simulator.



Batch file to run the simulation

- lab_01/src/lab1_hdl/simulation/01_simulate_with_modelsim.bat
- Creates a directory for temporary files, produced by ModelSim simulator
- Invokes the simulator executable *vsim*.
- *vsim* reads a stream of proprietary commands from a script file written in TCL (Tool Command Language).
- If you work under Linux, you can write a shell script that does the same.

```
rem recreate a temp folder for
rd /s /q sim
md sim
cd sim

rem start the simulation
vsim -do ../modelsim_script.tcl
```

TCL script file for ModelSim

- lab_01/src/lab1_hdl/simulation/modelsim_script.tcl
- TCL (pronounced "tickle" or tee cee el) is a scripting language used since 1990s in many EDA tools (EDA - Electronic Design Automation).
- You don't need to know it well, just copy somebody else's scripts for your projects.

```
# create modelsim working library
vlib work

# compile all the Verilog sources
vlog ../testbench.v ../../lab1.v

# open the testbench module for simulation
vsim -novopt work.testbench

# add all testbench signals to time diagram
add wave sim:/testbench/*

# run the simulation
run -all

# expand the signals time diagram
wave zoom full
```


Now run everything, modify the code and run again

The screenshot displays the ModelSim SE 10.2c environment. The left pane shows the Verilog code for a module named 'lab1'. The code defines two 1-bit inputs, KEY [1:0], and a 10-bit output, LED [9:0]. It implements several logic functions: basic AND, OR, and NOT gates; XOR gates for parity and control sum calculation; a NOT gate implemented using XOR with 1; and De Morgan law illustrations for LEDs 6, 7, 8, and 9.

```
1
2 module lab1
3
4     input [1:0] KEY, // KEYS
5     output [9:0] LED // LEDs
6
7
8     wire a = ~ KEY [0];
9     wire b = ~ KEY [1];
10
11     // Basic gates AND, OR and NOT
12     assign LED [0] = a & b;
13     assign LED [1] = a | b;
14     assign LED [2] = ~ a;
15
16     // XOR gates (useful for adders, compar
17     // parity and control sum calculation)
18     assign LED [3] = a ^ b;
19
20     // Building XOR only using AND, OR and
21     assign LED [4] = (a | b) & ~ (a & b);
22
23     // Building NOT by XORING with 1
24     assign LED [5] = a ^ 1'b1;
25
26     // De Morgan law illustration
27     assign LED [6] = ~ ( a & b ) ;
28     assign LED [7] = ~ ( a | ~ b ) ;
29     assign LED [8] = ~ ( a | b ) ;
30     assign LED [9] = ~ a & ~ b ;
31
32 endmodule
33
```

The right pane shows the waveform viewer, displaying the simulation results for the 'testbench/key' and 'testbench/led' signals. The 'testbench/key' signal is shown as a 2-bit bus with values 0 and 1. The 'testbench/led' signal is shown as a 10-bit bus with values 10'h003, 10'h0fe, and 10'h0da. The waveform viewer includes a toolbar, a search field, and a time axis ranging from 0 ns to 28 ns. A cursor is positioned at 10 ns.

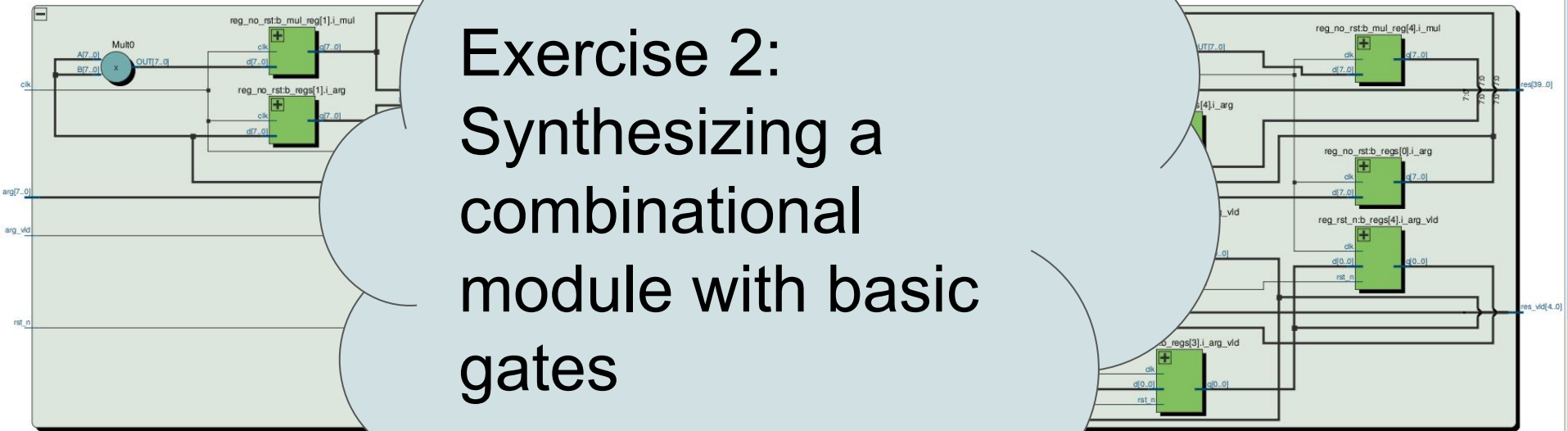Exercise 2: Synthesizing a combinational module with basic gates



The main Quartus project file

- lab_01/src/lab1_hdl/synthesis/lab1.qpf
- It is OK for the Quartus project file to be empty.
- Quartus usually stores some dates and versions there for Intel / Altera customer support.
- All the essential synthesis settings are not in .qpf, but in other files, .qsf and .sdc.

```
QUARTUS_VERSION = "17.0"  
DATE = "12:11:55 November 06, 2017"  
PROJECT_REVISION = "lab1"
```

TCL script with synthesis settings - 1

- lab_01/src/lab1_hdl/synthesis/lab1.qsf
- For this project you need only the four directives below, and some signal mapping assignments (see the next slide).
- You don't need to know all the script commands in the `.qsf` file.
- Just copy somebody's script and use the bare minimum settings.

```
set_global_assignment -name DEVICE 10M50DAF484C7G
set_global_assignment -name TOP_LEVEL_ENTITY lab1
set_global_assignment -name VERILOG_FILE ../../lab1.v
set_global_assignment -name PROJECT_OUTPUT_DIRECTORY .
```


TCL script with synthesis settings - 2

- lab_01/src/lab1_hdl/synthesis/lab1.qsf
- You need to map the port names in your design to the physical pins of the FPGA.
- The synthesis tool know the location of **PIN_B8** for chip **10M50DAF484C7G**, but it has no idea that the board connects it to a button and you call it KEY[0].

```
set_location_assignment PIN_B8 -to KEY[0]
set_location_assignment PIN_A7 -to KEY[1]
set_location_assignment PIN_A8 -to LED[0]
set_location_assignment PIN_A9 -to LED[1]
. . . . .
```

TCL script with synthesis settings - 3

- lab_01/src/lab1_hdl/synthesis/lab1.qsf
- Your .qsf file has to specify a so-called I/O standard for each signal connected to an FPGA pin.
- You don't need to know the meaning of the I/O standard property in this course.
- You can use wildcards for signal names when setting IO_STANDARD.

```
set_instance_assignment -name IO_STANDARD \  
    "3.3 V Schmitt Trigger" -to KEY*
```

```
set_instance_assignment -name IO_STANDARD "3.3-V LVTTTL" -to LED*  
. . . . .
```

Before synthesis create a copy of project files


- lab_01/src/lab1_hdl/synthesis/make_project.bat
- Intel / Altera Quartus Lite Edition creates a lot of temporary files
- It is convenient to run synthesis in a separate directory
- You have to copy project files into that directory
- To do this, run make_project.bat [Windows] / run make_project.sh

```
rd /s /q project
mkdir project
copy *.qpf project
copy *.qsf project
```

```
#!/bin/sh
rm -rf project
mkdir project
cp *.q[ps]f project
```

- File:Open Project
- Do not confuse with File:Open
- Find project file in your temporary project directory
- Do not open project from the original directory
- Double-click “Compile Design” in Tasks window

Run synthesis in Intel Quartus

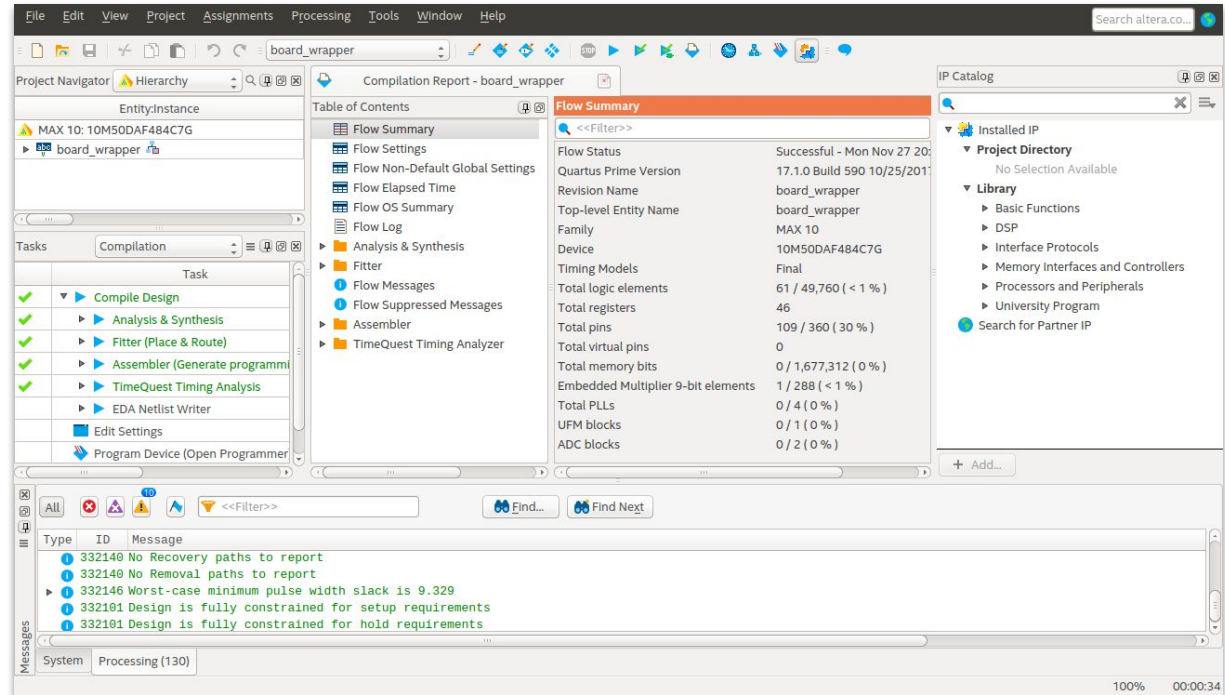


Netlist Navigator

top:1 +

top

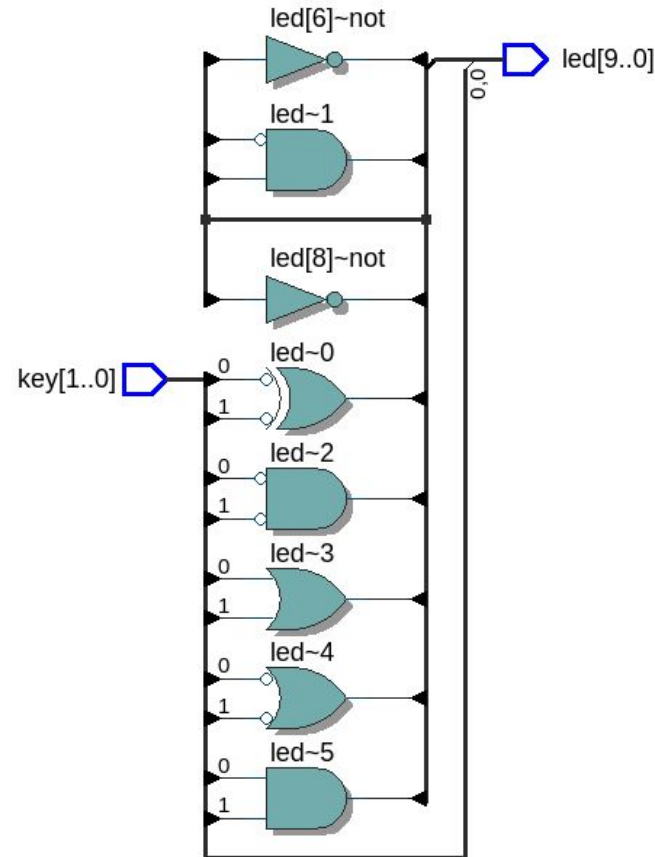- The task window menu has a viewer of FPGA-independent schematics.
- It shows the representation of your design after RTL analysis,
- but before mapping RTL to specific cells available in this particular FPGA




Netlist Navigator

top:1 +


top

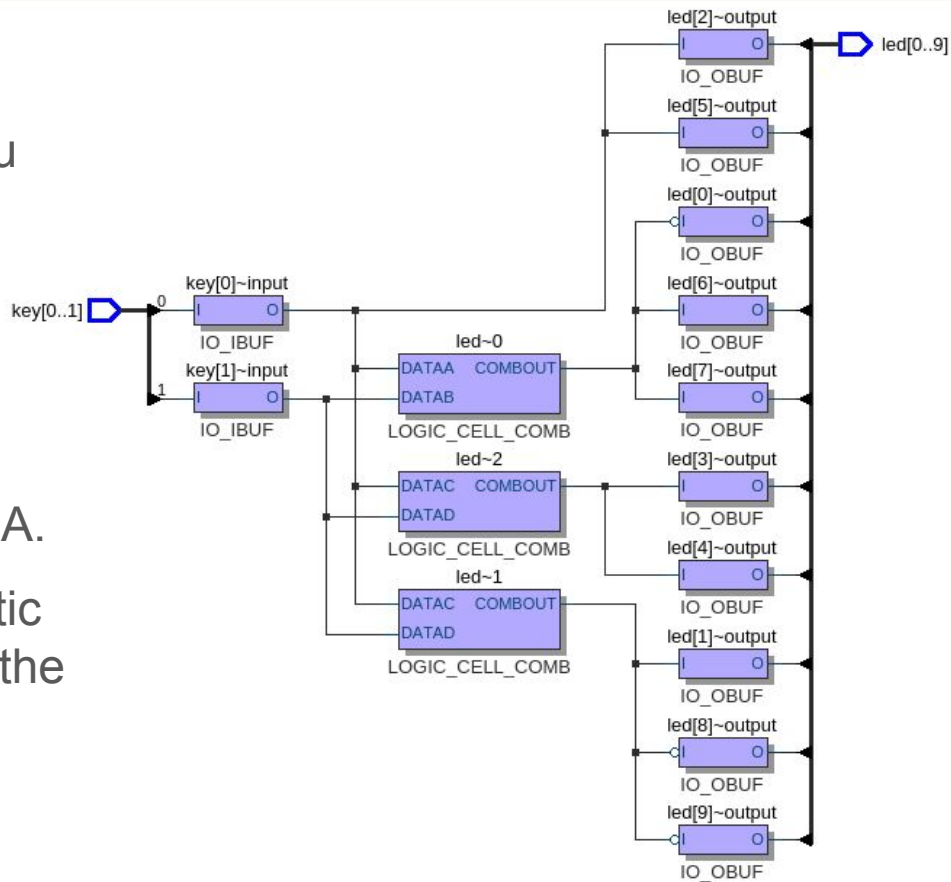- The task window menu also has a viewer of mapped schematics,
- where all your logic is mapped to blocks that directly correspond to cells in the target FPGA.
- Compare this schematic to the schematic from the previous slide.




Terasic DE10-Lite FPGA board

 - Inexpensive: \$85
- Academic price \$55
- Intel FPGA MAX 10 10M50DAF484C7G
- 50K cells, enough for designs with CPU cores like MIPSfpga
- On-board 64MB SDRAM
- Connects directly to PC for configuration



Configure FPGA on the board - 1

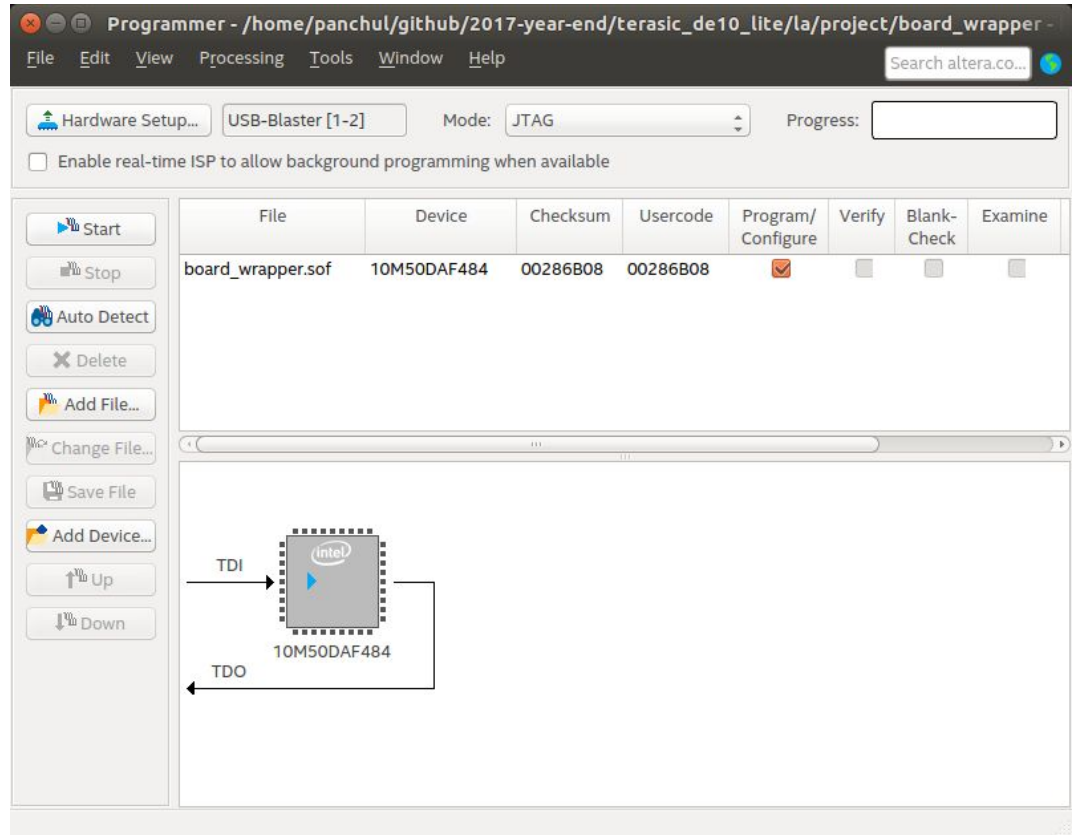- Find and click on “Program Device” in Tasks window
- Programmer window should appear
- If you see “USB-Blaster” next to “Hardware Setup”, the board is connected and found by software
- In this case just press “Start” button



Configure FPGA on the board - 2

- If you see “No hardware”, press “Hardware Setup”

The screenshot shows the Altera Programmer software interface. The title bar indicates the path: `/home/panchul/github/2017-year-end/terasic_de10_lite/la/project/board_wrapper`. The menu bar includes File, Edit, View, Processing, Tools, Window, and Help. A search bar for altera.co is visible in the top right.

The main interface displays a status bar with the following information:

- Hardware Setup... button
- No Hardware (selected)
- Mode: JTAG
- Progress: [Empty field]
- Enable real-time ISP to allow background programming when available


Below the status bar is a table with the following columns: File, Device, Checksum, Usercode, Program/Configure, Verify, Blank-Check, and Examine.

File	Device	Checksum	Usercode	Program/Configure	Verify	Blank-Check	Examine
board_wrapper.sof	10M50DAF484	00286B08	00286B08	<input checked="" type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>

Below the table is a diagram of the FPGA device, labeled "10M50DAF484", with an Intel logo. The diagram shows a TDI (Test Data In) input and a TDO (Test Data Out) output.


Configure FPGA on the board - 3

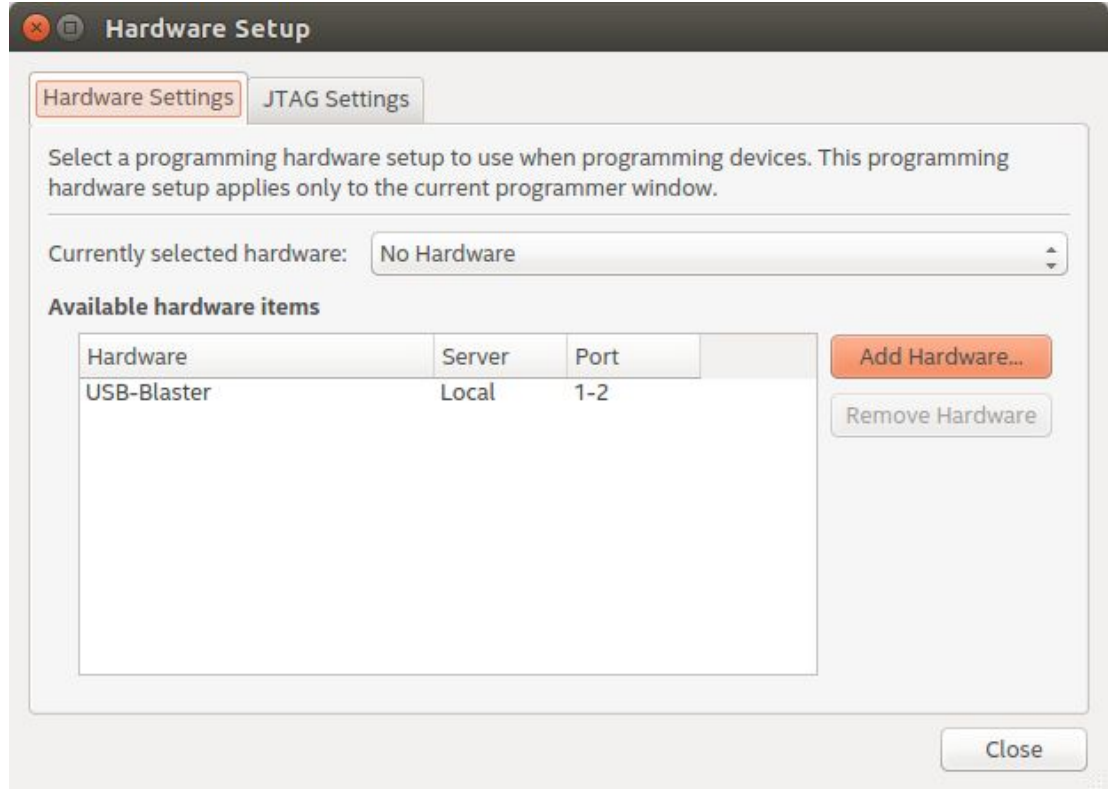- “Hardware Setup” window should appear with “USB-Blaster” listed under “Hardware”.
- If nothing is listed, check your USB cable connection.
- If the board is connected but nothing is listed, install USB-Blaster driver or resolve driver conflict.




Configure FPGA on the board - 4

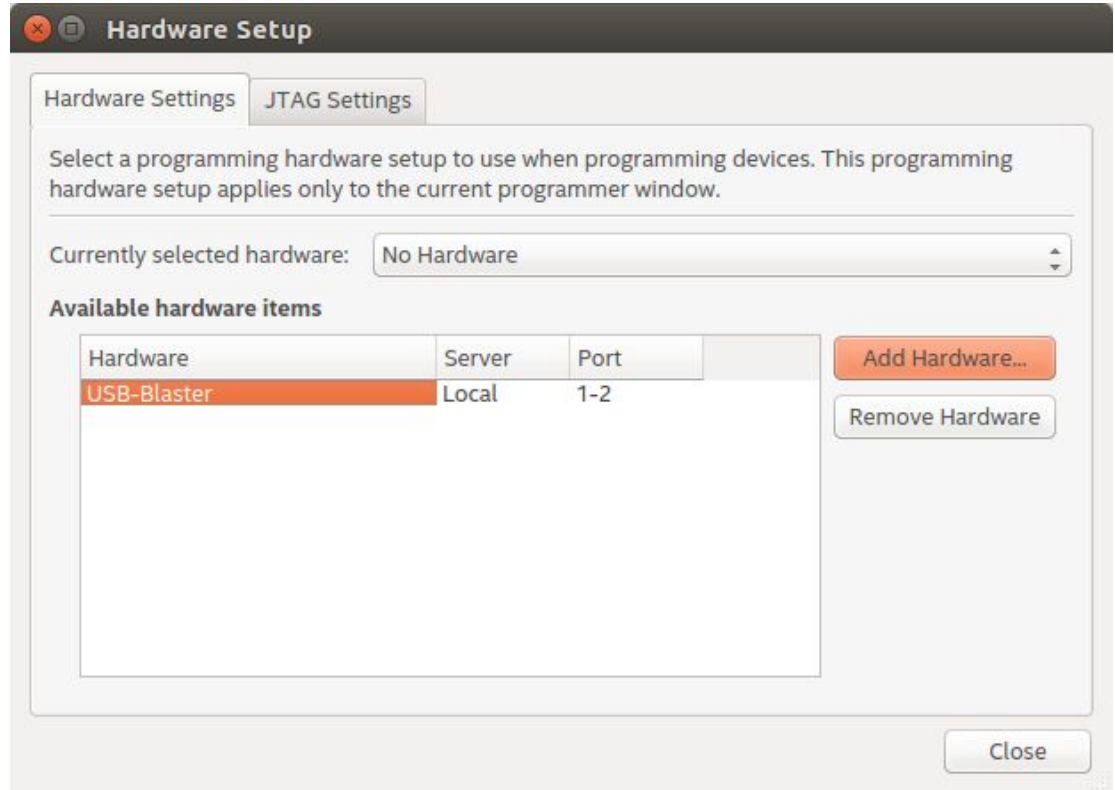- Double-click on “USB-Blaster”, then press “Close”




Configure FPGA on the board - 5

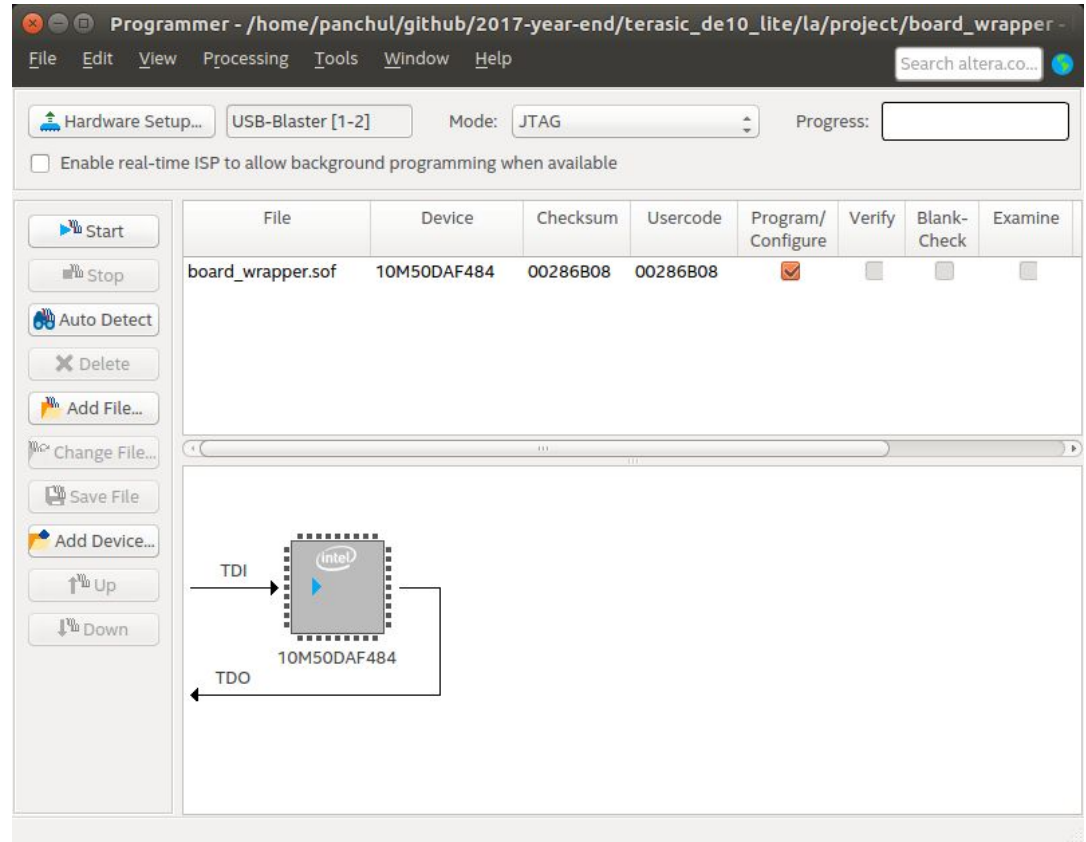- Now the hardware setup problem should be resolved
- Just press “Start” button and see the “Progress” indicator becoming green.
- If “Progress” gets stuck, unplug USB cable, plug it in again and repeat.



Add a new combinational element - MUX

 - Multiplexers, or muxes, implement the selection between values in hardware.
- The simplest way to infer mux in hardware is to use ternary `?:` operation.
- Modify the design with a mux, and re-run synthesis and FPGA configuration.





```
module mux_2_1
(
    input  [1:0] d0,
    input  [1:0] d1,
    input                sel,
    output [1:0] y
);

    assign y = sel ? d1 : d0;



endmodule
```

Add new signals to expand the design with MUXes

  - Two keys are not enough to demonstrate a mux because it is a ternary operation. You need to add new signals, connected to buttons and switches on the board
- Use the on-board 7-segment display to output digits or even letters
- Get the full .qsf file for DE10-Lite board from https://github.com/yuri-panchul/2017-year-end/tree/master/terasic_de10_lite




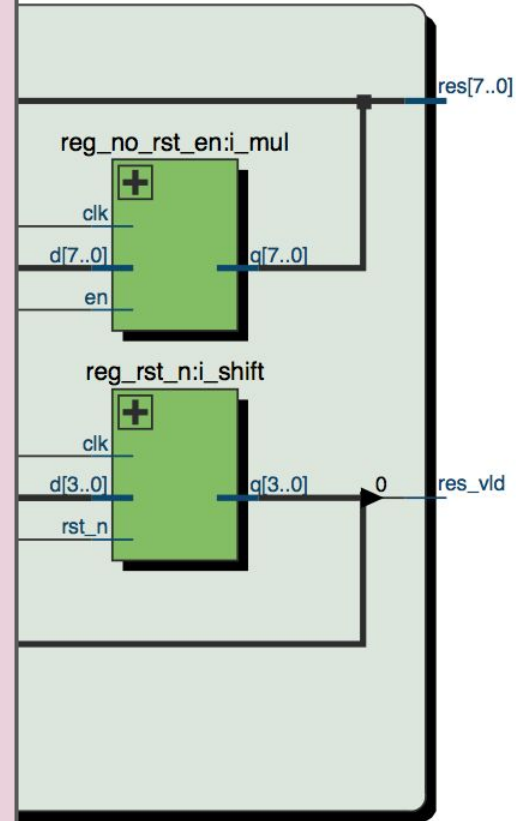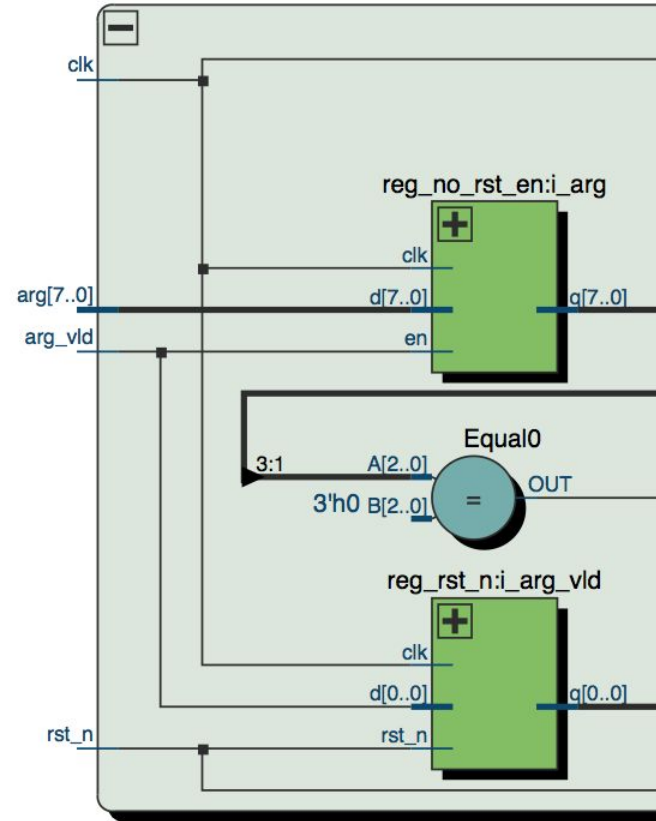Preview of the next Lab: Simulating and Synthesizing the Sequential Logic



Computation in combinational logic is not instant

 
- It takes time for an electric signal to propagate.
- Before the results are ready, the outputs may contain random values.
- How to find when the results are ready?
- We can synchronize the computations with a special signal called clock.




The picture is from Digital Design and Computer Architecture, 2nd Edition by David Harris and Sarah Harris. Elsevier, 2012

Clocks are useful not only to synchronize outputs

 - Circuits synchronized with clocks are called sequential.
- Sequential circuits can also have memory and perform iterative computations.
- We will learn about sequential circuits in Lab 2.



 

Thank You!

