
 




# HDL, RTL and FPGA: Lab 2

Review of your next steps  
in designing digital hardware

Marker: 670 ns | Cursor: 290500 ps

 

Refreshing knowledge from Lab 1

 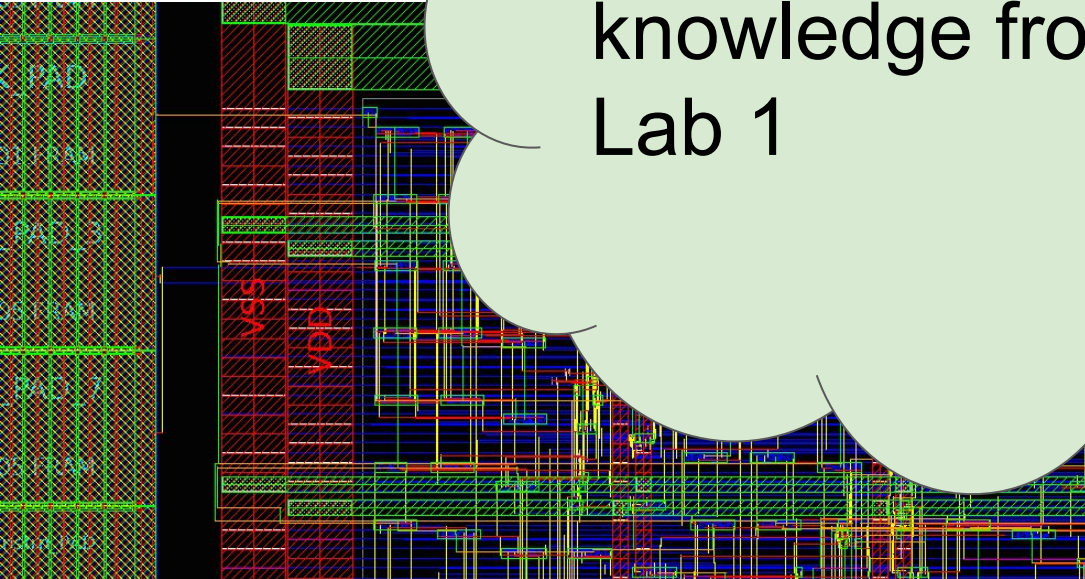

1651F3



# Software: from C to processor instructions

**C:**

```
int f (int a, int b)
{
    int s = 0;

    while (s < a)
        s += b;

    return s;
}
```



**Assembly:**

```
                .set noreorder
sum:
    blez        $4, exit
    move       $2, $0

    addu       $2, $2, $5

loop:
    slt        $3, $2, $4
    bnel       $3, $0, loop
    addu       $2, $2, $5

exit:
    jr         $31
    nop
```



**Machine code**

```
18800005
00001025



00451021

0044182a
5460fffe
00451021

03e00008
00000000
```
  
# Circuits: from Verilog to transistors (simplified)

```
module counter
(
  input clock,
  input reset,
  output logic [1:0] n
);
always @(posedge clock)
begin
  if (reset)
    n <= 0;
  else
    n <= n + 1;
end
endmodule
```




# What is an FPGA? A simplified explanation

A matrix of cells with changeable function

One cell can become AND, another OR, yet another - one bit of memory

An FPGA does not contain a fixed CPU, but can be configured to work as a CPU

 A picture from <http://jjmk.dk/MMMI/PLDs/FPGA/fpga.htm>




**IOB**  
Input Output Block


**CLB**  
Configurable  
Logic Block

**PSM**  
Programable  
Switch Matrix


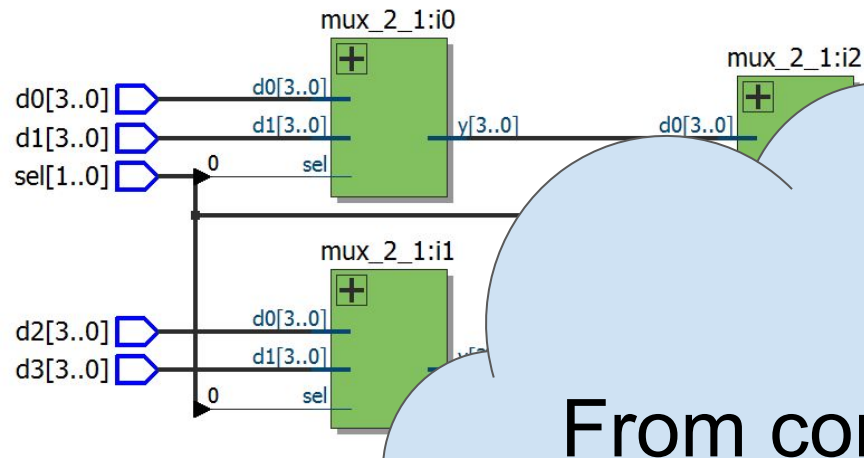
**Connection lines**  
Single, Long  
Double, Direct



Marker: 670 ns | Cursor: 290500 ps

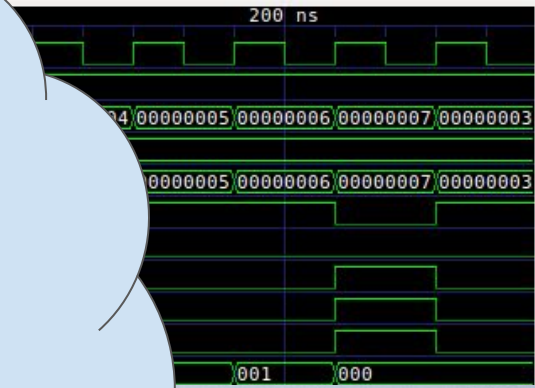


From combinational  
to sequential logic

  
 
# From Lab 1: Combinational logic

- The outputs of the group of components depend only on inputs
- You set inputs and get outputs after some time
- This group is called “a combinational cloud”
- Used to calculate logic and arithmetic functions



```
module top
(
    input  a, b, c, d,
    output e, f
);


    assign e = a & (b | c);
    assign f = ~ (c ^ d);

endmodule
```


 
# Computation in combinational logic is not instant



- Before the results are ready, the outputs may contain random values.
- How to find when the results are ready and can be used by the next step of computation?
- We can synchronize the computation with a special signal called clock.



The picture is from Digital Design and Computer Architecture, 2nd Edition by David Harris and Sarah Harris. Elsevier, 2012

  
# Clock is a periodic signal with square waveform

- This period is long enough for any combinational computation to complete.
- Clock frequency =  $1 / \text{period}$ .
- Clock is usually generated by a crystal oscillator (find it on the board).



 
# A circuit synchronized with a clock is called sequential

- The sequential circuit go through a sequence of states.
- The current state is stored in D-flip-flops.
- A new state is computed based on the previous state and the circuit's inputs.
- A new state is recorded into D-flip-flops when clock goes from low to high.
- The outputs are computed based on the inputs and the current state




# Huffman model of sequential circuits

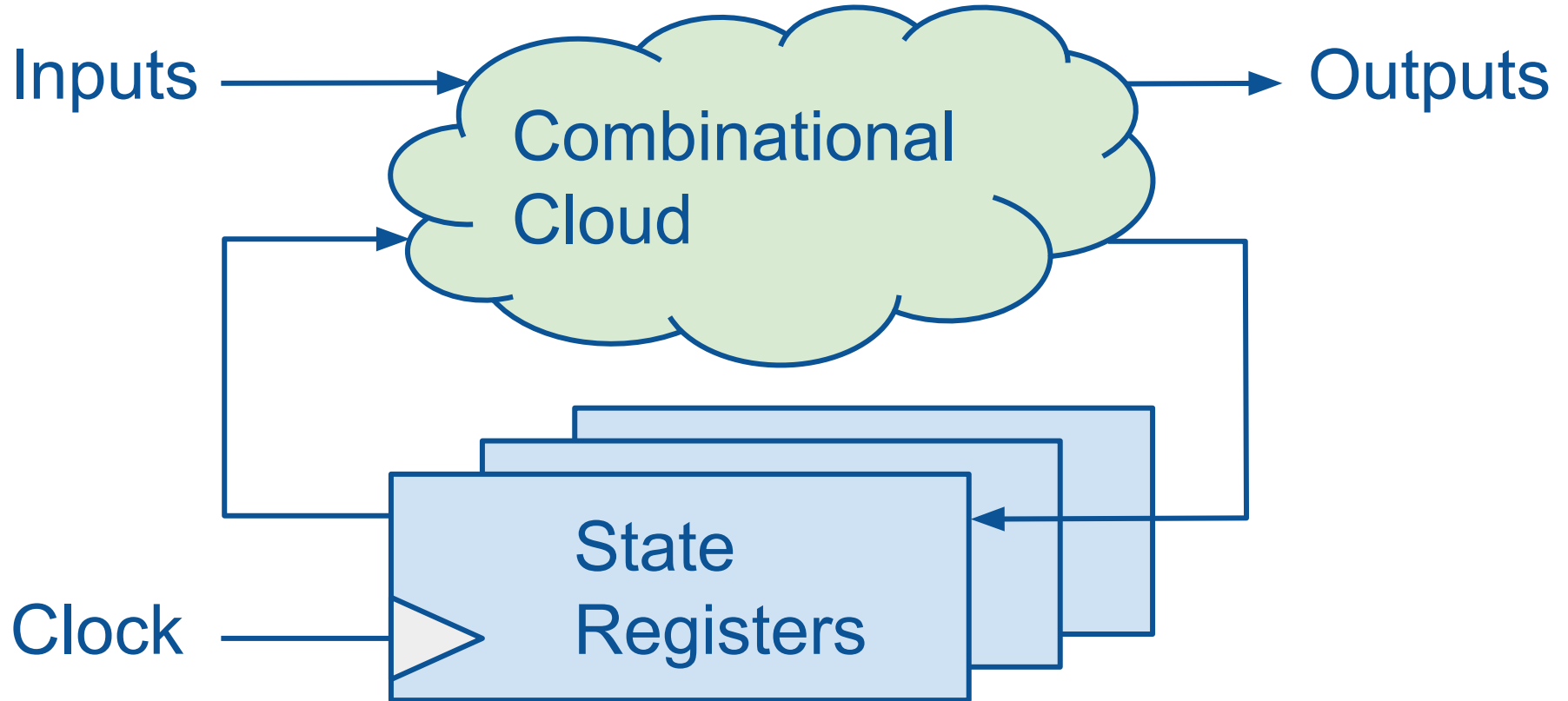


 
# What the sequential logic allows us to do

- Counting
- Memorizing the information
- Adding new data and repeating the computation
- Waiting for an event coming from outside the device
- In short: sequential logic is what makes a computer to do interesting things





A picture of John Searle's Chinese room thought experiment is from <http://deskarati.com/2014/07/01/john-searles-chinese-room-thought-experiment>

Marker: 670 ns | Cursor: 290500 ps

  

# The Exercises

  

# Lab 2 exercises

1. The function of a D-flip-flop, the basic brick of a sequential design
2. Counter, a combination of combinational and sequential
3. Connecting flip-flops back-to-back to make a shift register
4. Finite State Machine (FSM) for sequence recognition
5. The application of FSM for interfacing sensors
6. The concept of pipelining
7. Looking forward schoolMIPS and MIPSfpga

# D-flip-flop records the data at the end of clock cycle

- “Always at positive edge of `clk` store the value of signal `d` in a D-flip-flop inferred by variable `q`. `q` is also connected to the output”.
- `always` block is similar to the `initial` block, however it is evaluated on every event described after `@`.
- The assignment `<=` is called non-blocking, it will take effect after all current `always` blocks get evaluated

```
module d_flip_flop
(
    input    clk,
    input    d,
    output   reg q
);

always @ (posedge clk)
    q <= d;
```



# Reset signal guarantees the initial state

- This design uses reset active low (“`negedge rst_n`”), some others use reset active high.
- Reset is necessary for control signals, so the device does not act erratically on power-up.

```
module dff_async_rst_n
(
    input        clk,
    input        rst_n,
    input        d,
    output reg   q
);


always @ (posedge clk or negedge rst_n)
    if (!rst_n)
        q <= 0;
    else
        q <= d;
```

A group of D-flip-flops is called a register.



- Do not confuse with Verilog `reg` or CPU registers in programming.
- We can parameterize the number of D-flip-flops in a register using Verilog `parameter` declaration.

```
module dff_async_rst_n_param
#(
    parameter WIDTH = 8,
           RESET = 8'b0
)
(
    input                clk,
    input                rst_n,
    input [WIDTH - 1 : 0] d,
    output reg [WIDTH - 1 : 0] q
);
```



 
# Register keeps the value during the cycle


 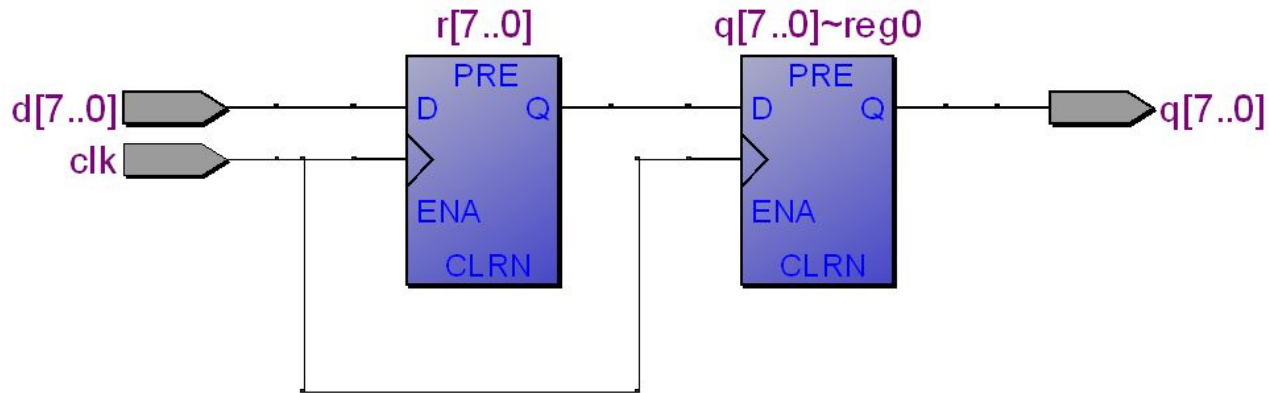
# Two registers back-to-back delay for two cycles



# Compare

   

# Generating and using clock in a testbench

You can also use clock to schedule assigning stimuli, the values for the DUT ports (DUT = Design under Test).

```
initial
begin
    clk = 0;

    forever
        # 10 clk = ! clk;
end
```

```
initial
begin
    clk_en  <= 1'b1;
    arg_vld <= 1'b0;


    repeat (2) @ (posedge clk);
    rst_n <= 0;
    repeat (2) @ (posedge clk);
    rst_n <= 1;
end
```

# Adder + Register = Counter

- A group of D-flip-flops is called a register.
- Do not confuse with Verilog `reg` or CPU registers in programming.
- In this code the result of addition is stored to use in the next clock cycle.


```
module counter
(
    input          clock,
    input          reset_n,
    output reg [31:0] count
);

 
always @(posedge clock or negedge reset_n)
begin
    if (!reset_n)
        count <= 32'b0;
    else
        count <= count + 32'b1;
end
```



 
The register contains 0, it gets propagated to the adder.






 

 
0 enters the adder. The adder's output is not stable yet.



 
The adder computed  $0 + 1 = 1$ . Register still contains 0.



 
Positive edge of the clock is coming. Register is still 0.



 
The aperture time. Register is about to store 1.



 The register recorded 1 and is about to propagate it outside.




 The current state is 1, it gets propagated to the adder.




 1 enters the adder. The adder's output is not stable yet.






 
The adder computed  $1 + 1 = 2$ . The register still contains 1.



 
A positive edge of the clock is coming. The register is still 1.



 
The aperture time. The register is about to store 2.



 The register recorded 2 and is about to propagate it outside.




 The current state is 2, it gets propagated to the adder.



 
# Finite State Machine, the decision maker

- Let's implement an example of FSM that recognizes sequences.
- We got this example from Digital Design and Computer Architecture by David Harris and Sarah Harris, 2012.
- “A snail crawls down a paper tape with 1's and 0's on it. The snail smiles whenever the last two digits it has crawled over are 01. Design a state machine of the snail's brain.”
- An FSM is a special case of a Huffman sequential circuit.
- Mealy FSM uses inputs directly to compute outputs, Moore's FSM does not.




# FSM designers use state transition diagrams

## Moore FSM

 

## Mealy FSM

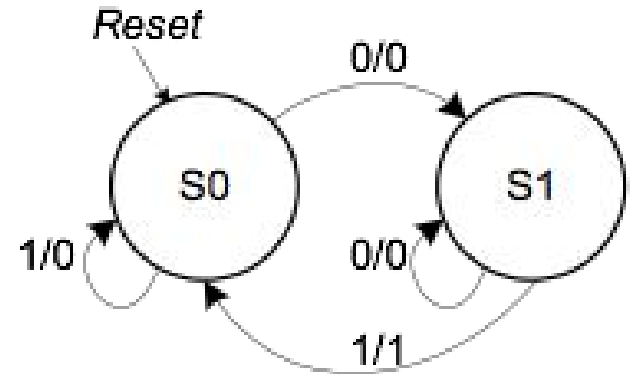

- Circles designate states.
- Arcs designate transitions depending on inputs.
- For Mealy FSM arcs indicate inputs / outputs.



# Coding FSMs in Verilog - State register

```
module pattern_fsm_moore
(
    input  clock,  input  reset_n,
    input  enable, input  a,  output y
);

parameter [1:0] S0 = 0, S1 = 1, S2 = 2;
reg [1:0] state, next_state;

// State register
always @ (posedge clock or negedge reset_n)
    if (! reset_n)
        state <= S0;
    else if (enable)
        state <= next_state;
```

# Coding FSMs in Verilog - Next state logic

```
// Next state logic
```



```
always @*  
    case (state)  
    S0: if (a) next_state = S0; else next_state = S1;  
    S1: if (a) next_state = S2; else next_state = S1;  
    S2: if (a) next_state = S0; else next_state = S1;  
    default: next_state = S0;  
    endcase
```

```
// Output logic based on current state
```


```
assign y = (state == S2);
```
  
# Examples: interfaces to sensors

- Ultrasonic distance sensor
  - [https://github.com/yuri-panchul/2017-year-end/blob/master/terasic\\_de10\\_lite/hc\\_sr04\\_receiver.v](https://github.com/yuri-panchul/2017-year-end/blob/master/terasic_de10_lite/hc_sr04_receiver.v)
- Digilent Ambient Light Sensor with SPI protocol
  - [https://github.com/yuri-panchul/2017-tomsk-novosibirsk-astana/blob/master/parts\\_and\\_examples/pmod\\_als\\_spi\\_receiver/pmod\\_als\\_spi\\_receiver.v](https://github.com/yuri-panchul/2017-tomsk-novosibirsk-astana/blob/master/parts_and_examples/pmod_als_spi_receiver/pmod_als_spi_receiver.v)




 Synthesis tools recognize FSMs and optimize them



 
# The concept of pipelining - 1

- Suppose we have a computation that consists of multiple steps.
- We can compute a new set of data each clock cycle.
- The clock has a period of  $t_{FGH}$ .



 
# The concept of pipelining - 2

- We add registers between the steps.
- It reduces the clock period from  $t_F + t_G + t_H$  to  $\max(t_F, t_G, t_H)$ .
- Now we can put a new set of inputs before the results for the previous sets went all the way  $F \rightarrow G \rightarrow H$ .
- The throughput of the module increases.



 
# The concept of pipelining - 3

- An application of the pipelining principle for computing  $F(n) = n^5$ .
- We put a new input each cycle and get the result 4 cycles later.


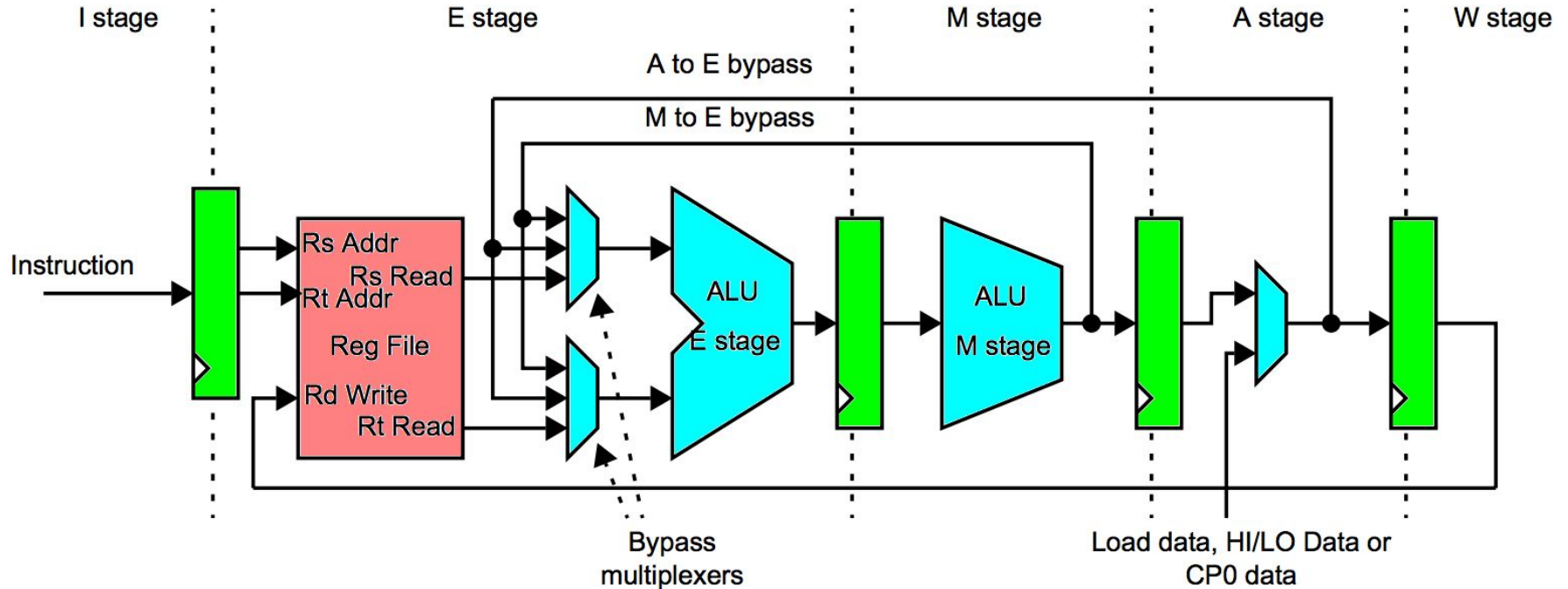
# CPU pipeline, best-known example of the pipelining principle


The execution unit of MIPS M5150 CPU core processes the stream of instructions




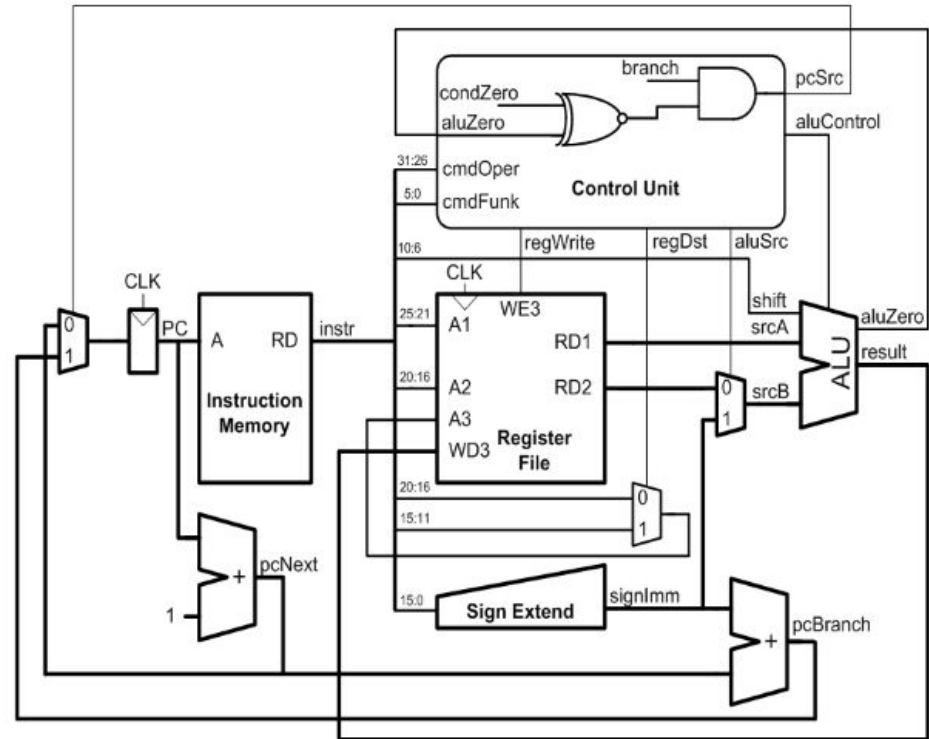
# Learn about CPUs using schoolMIPS and MIPSfpga

- schoolMIPS is as simple RISC CPU as you can get, use it to learn the basics.
- MIPSfpga is to experiment with an industrial core, it uses a variant of MIPS M5150 from the previous slide



Thank  
You!

